

Computer Organization

Multi-cycle CPU

Gyuhyeon Lee (guhylee@snu.ac.kr)

High Performance Computer System (HPCS) Lab

April 13, 2017

Objective

- To implement a multi-cycle CPU, which supports full TSC ISA.


Details of Objective

- To design a datapath & a control unit of the multi-cycle CPU
- You are free to revise your previous (single-cycle) CPU, or design it from scratch.

Full TSC supports

- Please refer to the **[Assn4] tsc_ISA.rev.1.pdf** file.
 - The previous one has lots of typos, so I revised it.

Control unit of Multi-cycle CPU

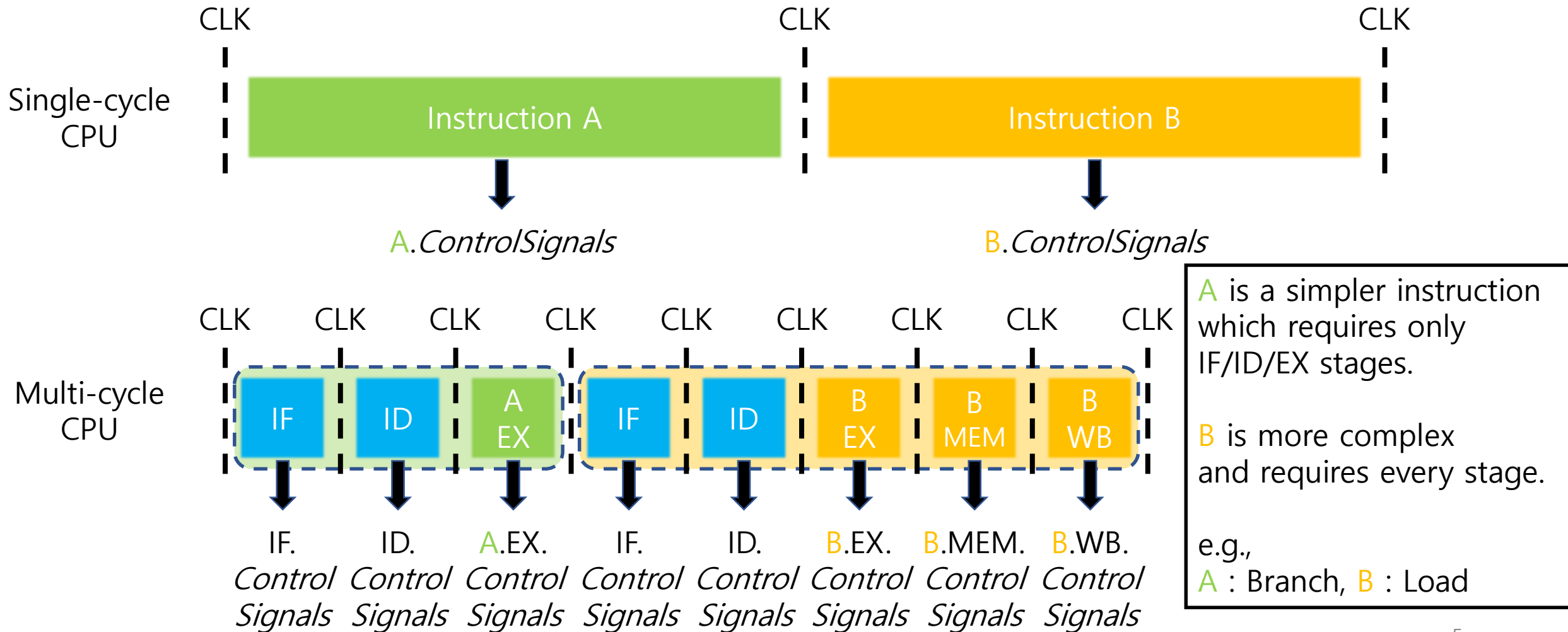


Control unit of Multi-cycle CPU




The execution starts from the IF stage.

Control unit of Multi-cycle CPU

 


Then, it shifts to the ID stage.

Control unit of Multi-cycle CPU

 


These two stages are universal,
because it doesn't know the type of instruction yet.

Control unit of Multi-cycle CPU

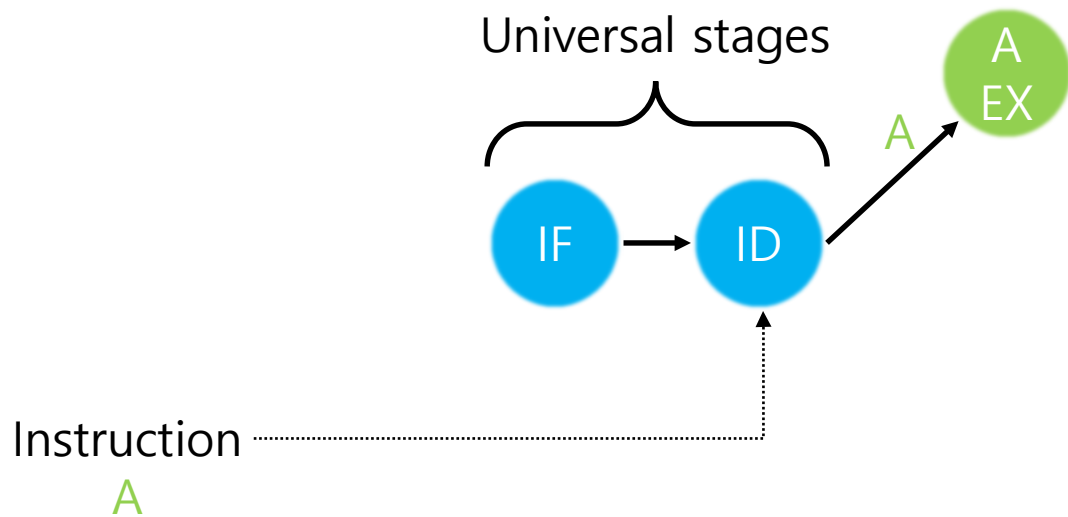


After decoding, it realizes the instruction type.
Let's assume that the instruction is **A**.

Control unit of Multi-cycle CPU

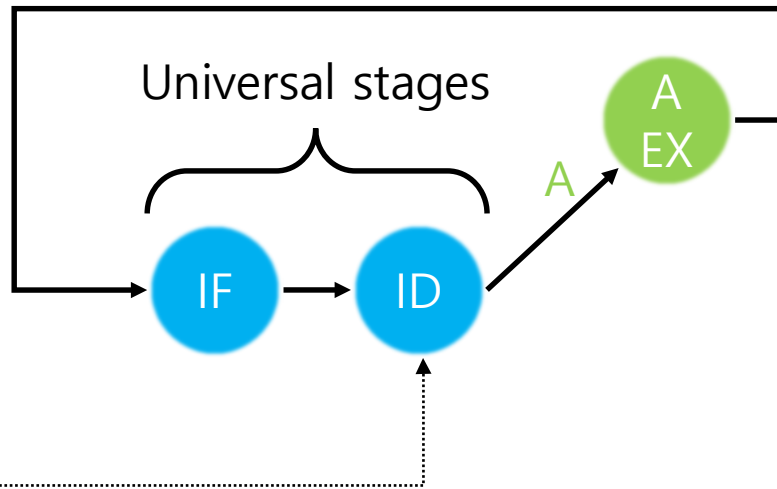


After it finishes execution, it has to return to the IF stage.

Control unit of Multi-cycle CPU

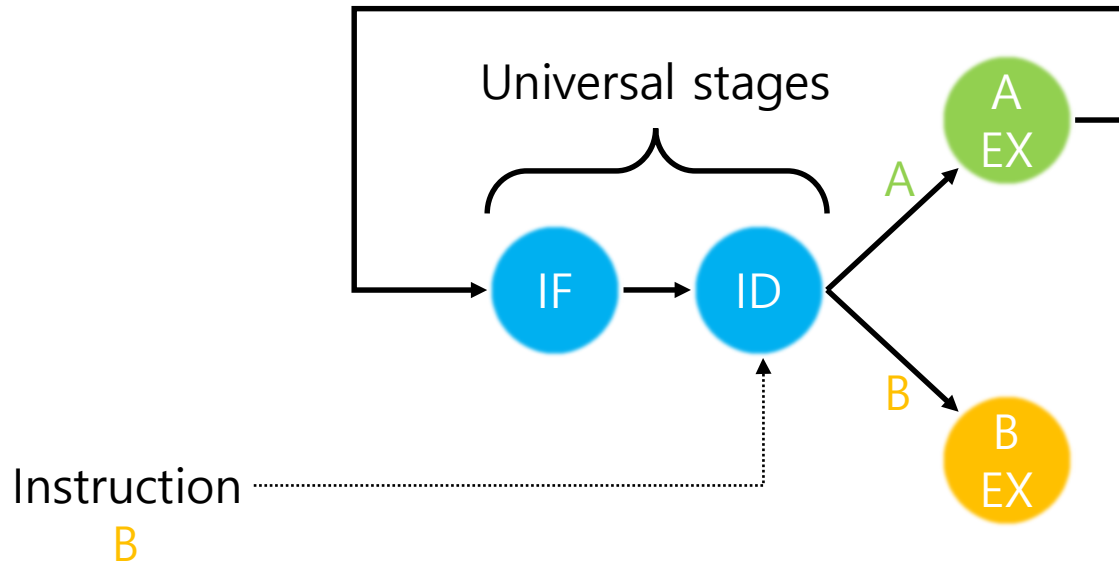


Let's assume that the next instruction is B

Control unit of Multi-cycle CPU

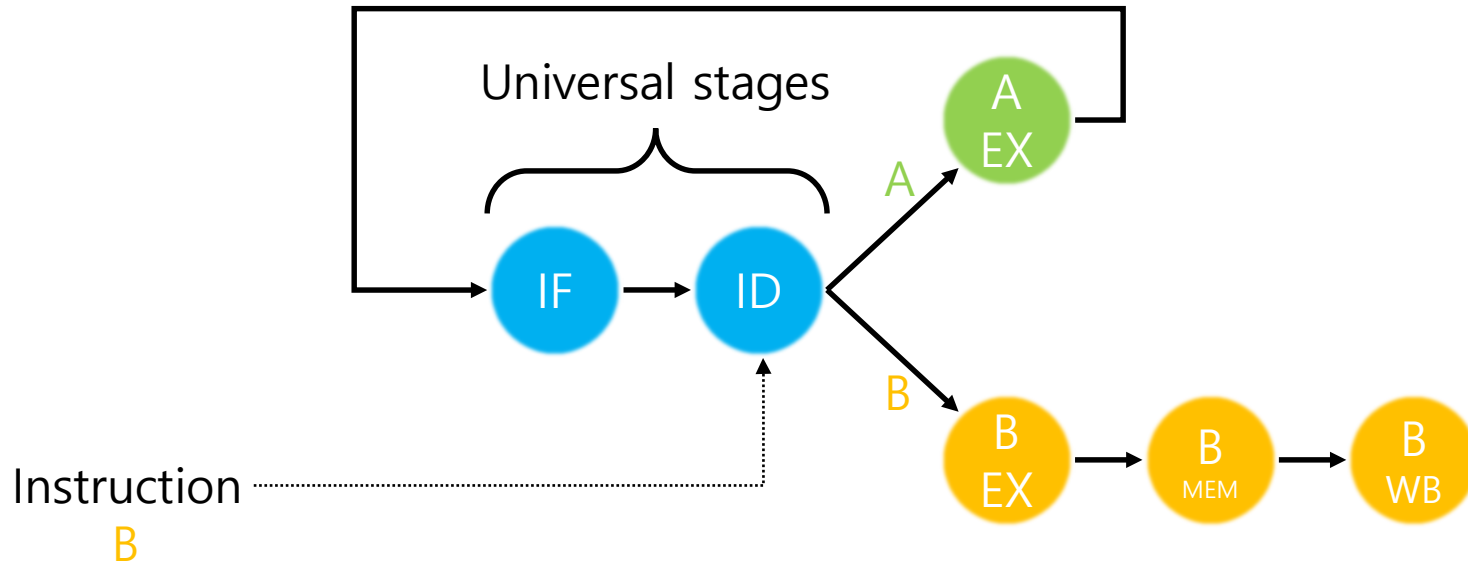


The instruction **B** requires the MEM and WB stage.

Control unit of Multi-cycle CPU

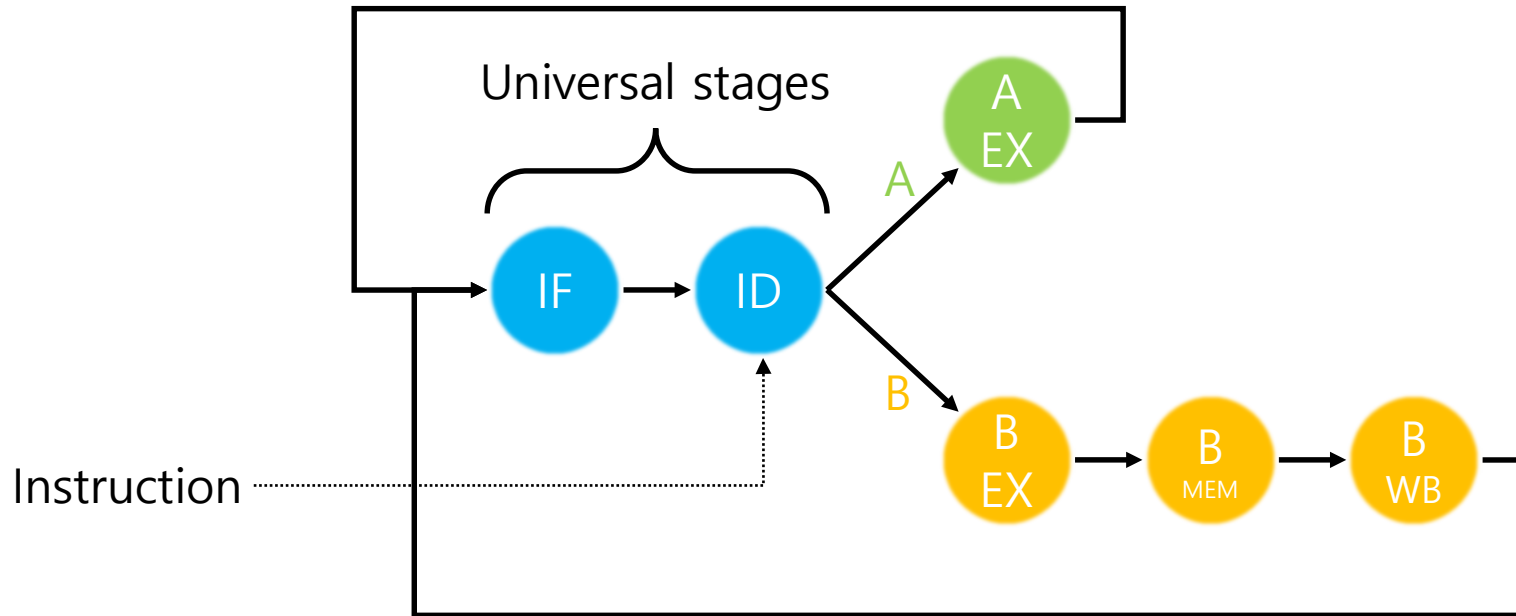


After it finishes execution, it also has to return to the IF stage.

Control unit of Multi-cycle CPU

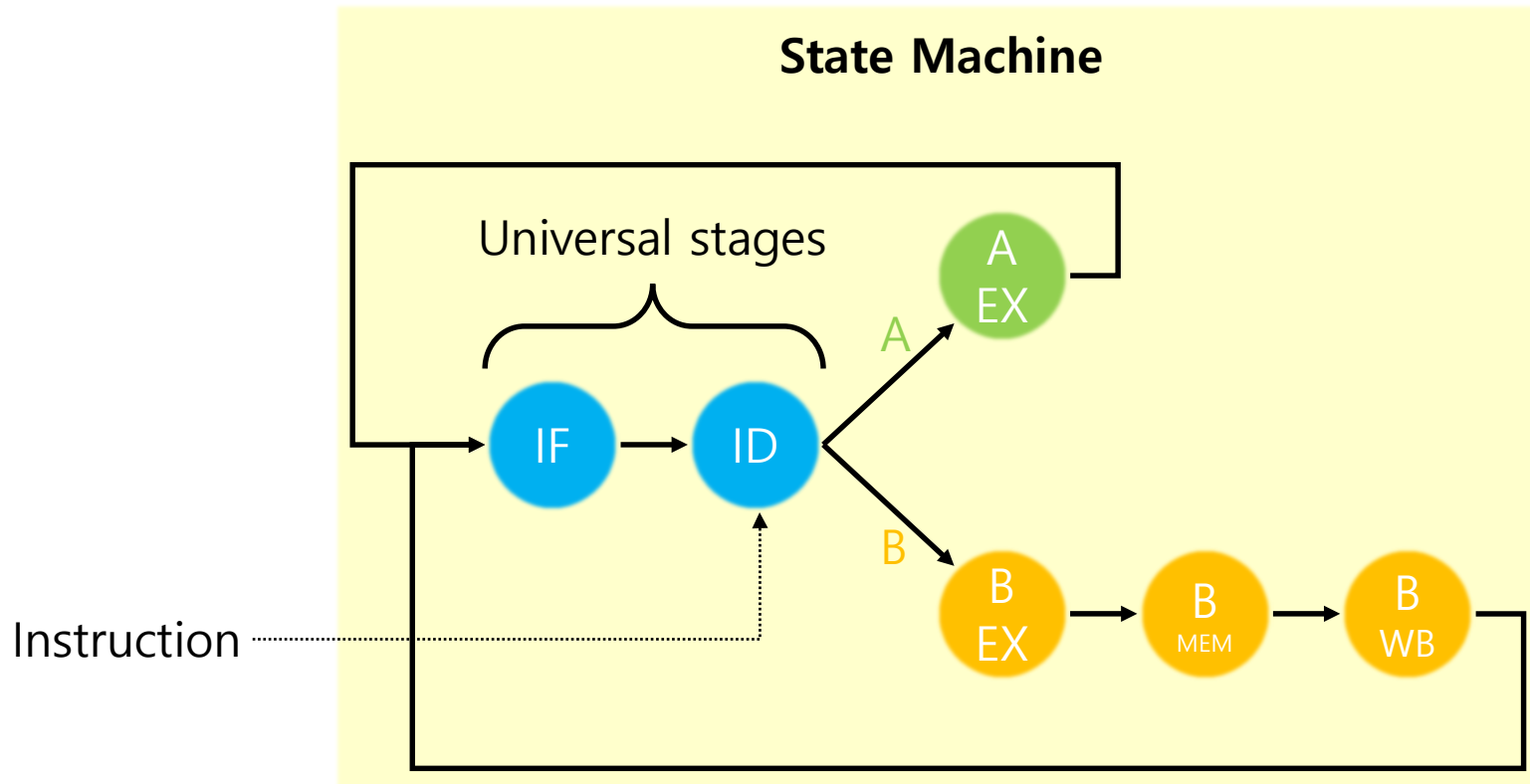


All of these stages form the state machine for the control unit.

Control unit of Multi-cycle CPU

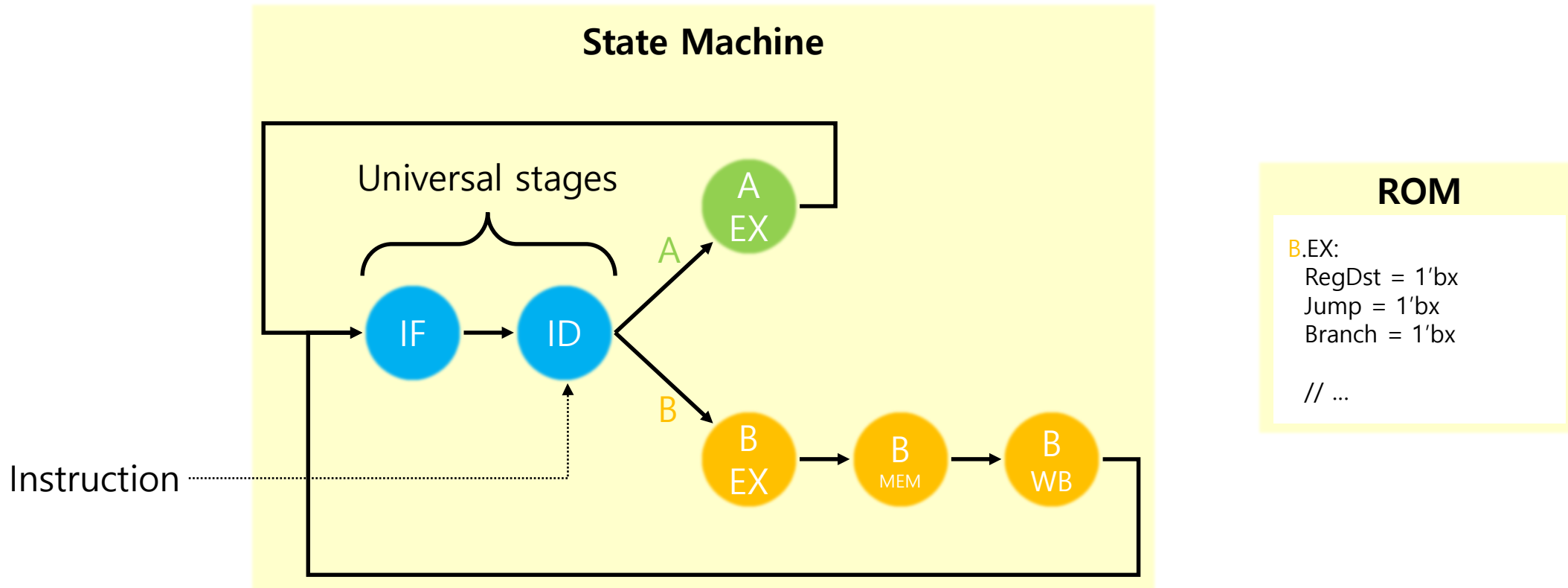


The control signals for each stage are stored in the ROM.

Control unit of Multi-cycle CPU

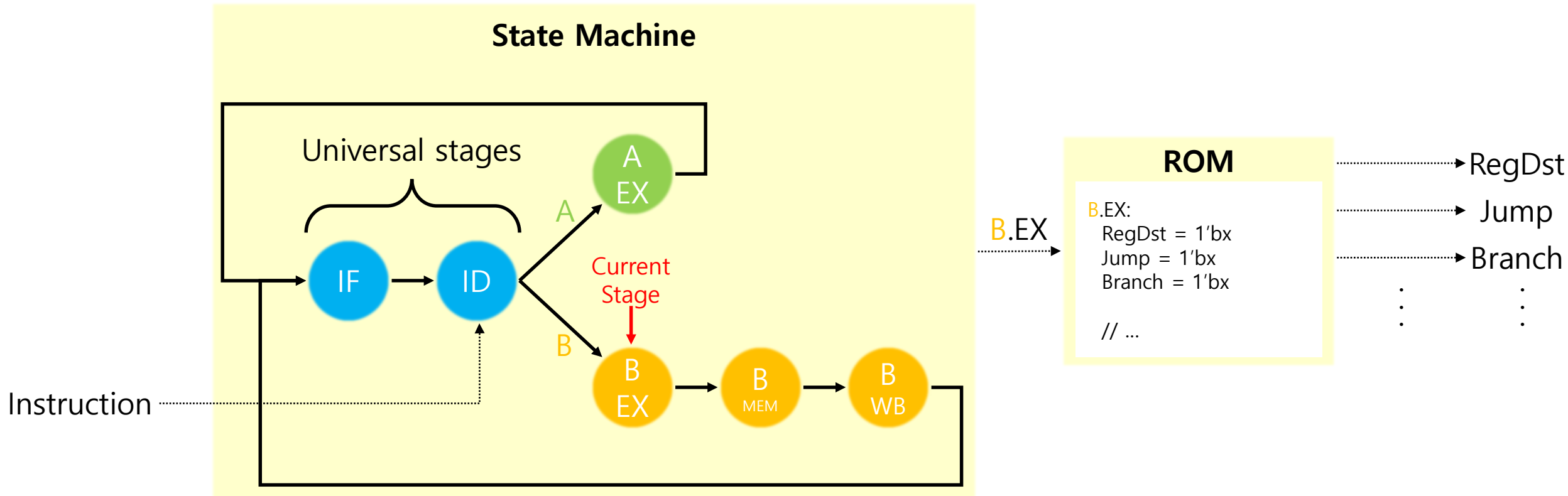

The ROM outputs the control signals for the current stage.

Control unit of Multi-cycle CPU

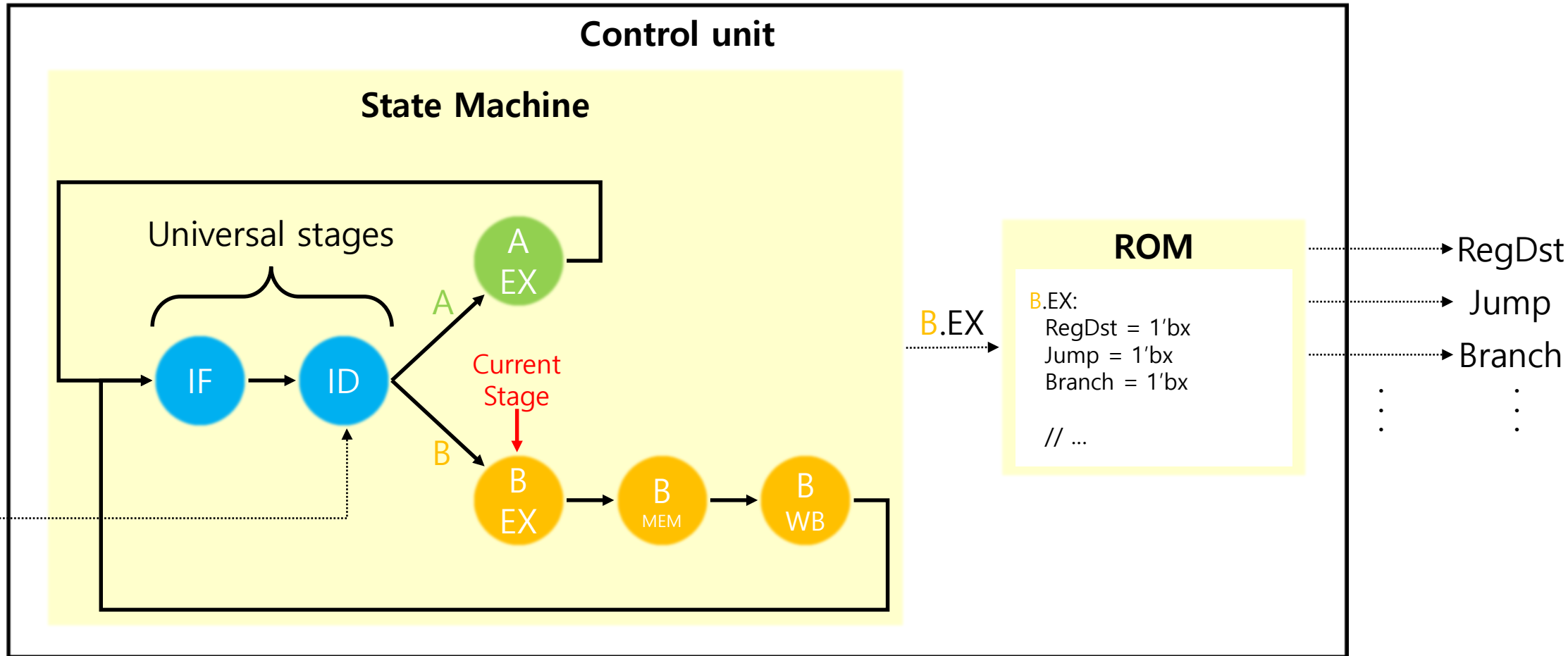


Put these structures together to build a control unit.

Datapath of Multi-cycle CPU

- You may need to revise your ALU:
 - You may want to add some opcodes:
 - e.g., comparing two integers
 - You may want to add another port:
 - e.g., an output port for the result of comparison
 - You may want to remove useless opcodes & ports:
 - e.g., rotate left/right opcodes, Cin/Cout ports
- You can freely revise your previous ALU.

Datapath of Multi-cycle CPU

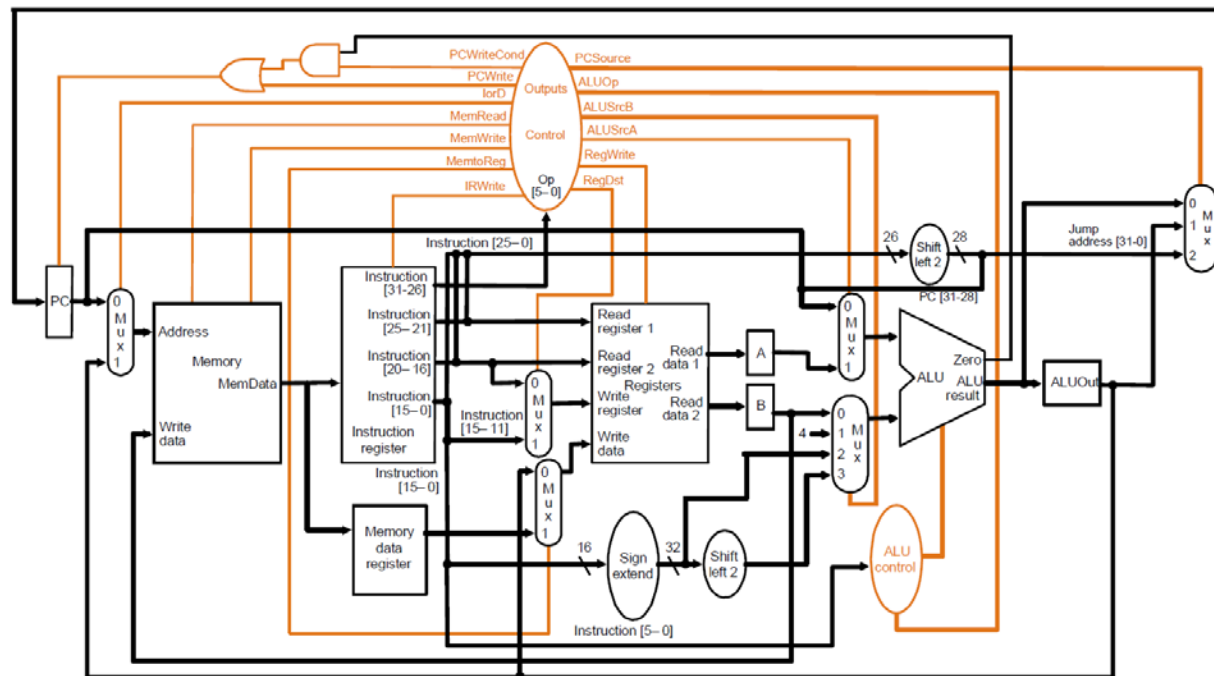- Your datapath must be capable of executing all TSC instructions.
- The lecture note for the multi-cycle CPU will be the best reference.
 - However, you can do what you want, as long as it works.



CPU-Memory interface


- Your CPU has to support Load/Store instructions.
- **PLEASE BE CAUTIOUS:** I revised the memory code.

```
// model the read process
assign data = readM ? outputData : `WORD_SIZE'bz;
always begin
    inputReady = 0;
    outputData = `WORD_SIZE'bz;
    #`PERIOD1;
    forever begin
        wait (readM == 1);
        #`READ_DELAY;
        outputData = memory[address];
        inputReady = 1;
        wait (readM == 0);
        outputData = `WORD_SIZE'bz;
        inputReady = 0;
    end // of forever loop
end // of always block for memory read
```


```
// model the write process
always begin
    #`PERIOD1;
    forever begin
        wait (writeM == 1);
        #`WRITE_DELAY;
        memory[address] = data;
        wait (writeM == 0); // wait for write pulse to go back to 0
    end // of forever loop
end // of always block for memory write
```

- I removed the “Stable Time”, so *data* keeps its value until you turn the *readM* signal off.

CPU-Memory interface

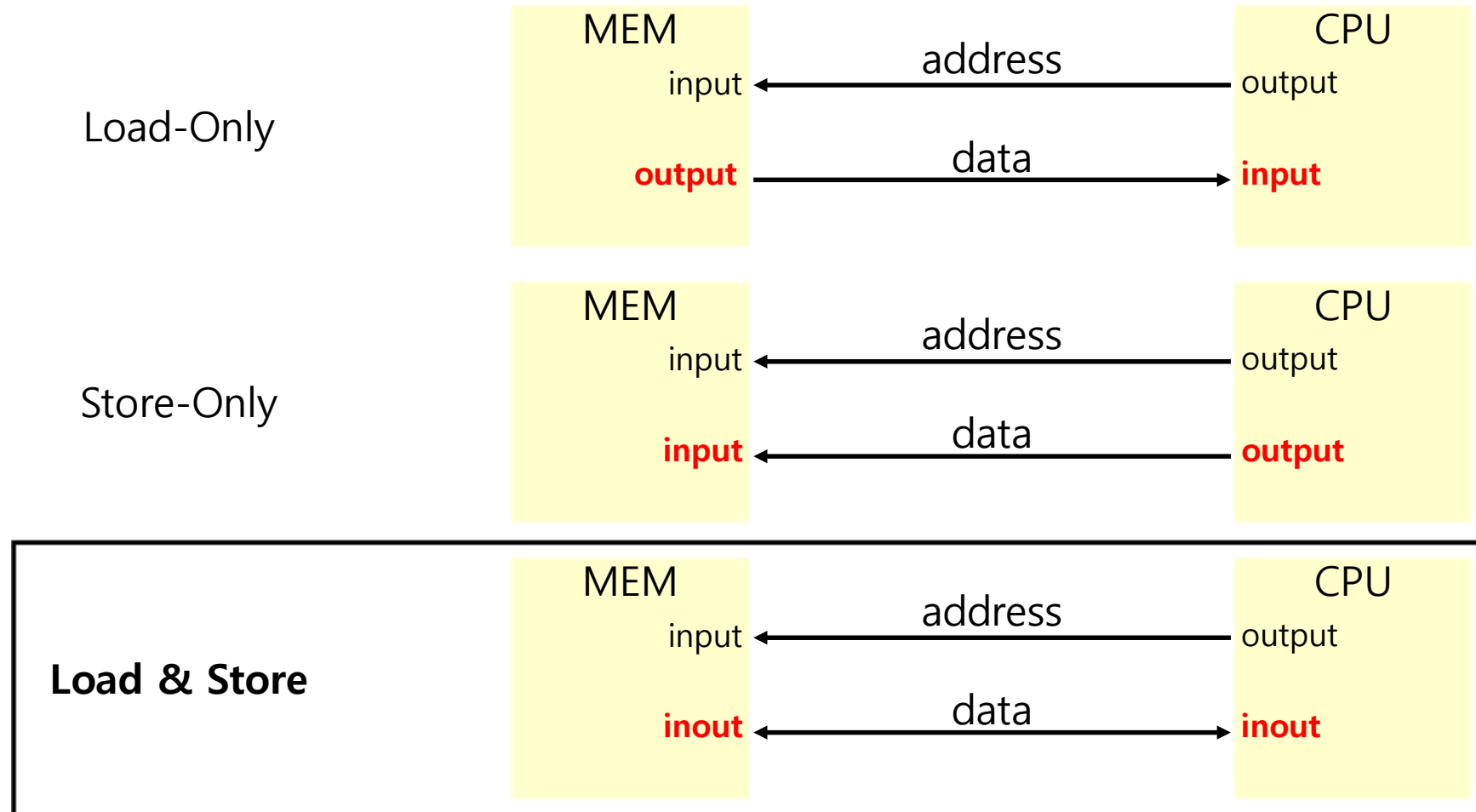


CPU-Memory interface

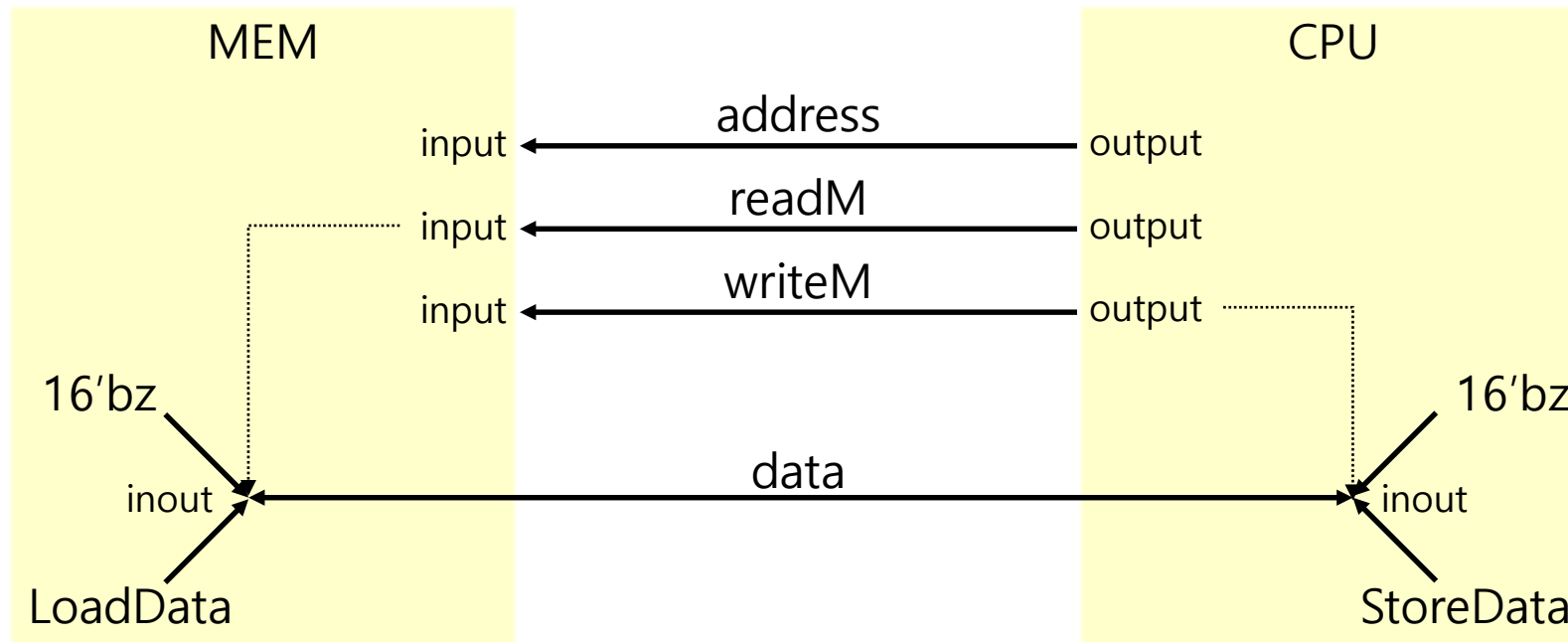


'z', a high-impedance state, is a special bit value.

CPU-Memory interface – Load

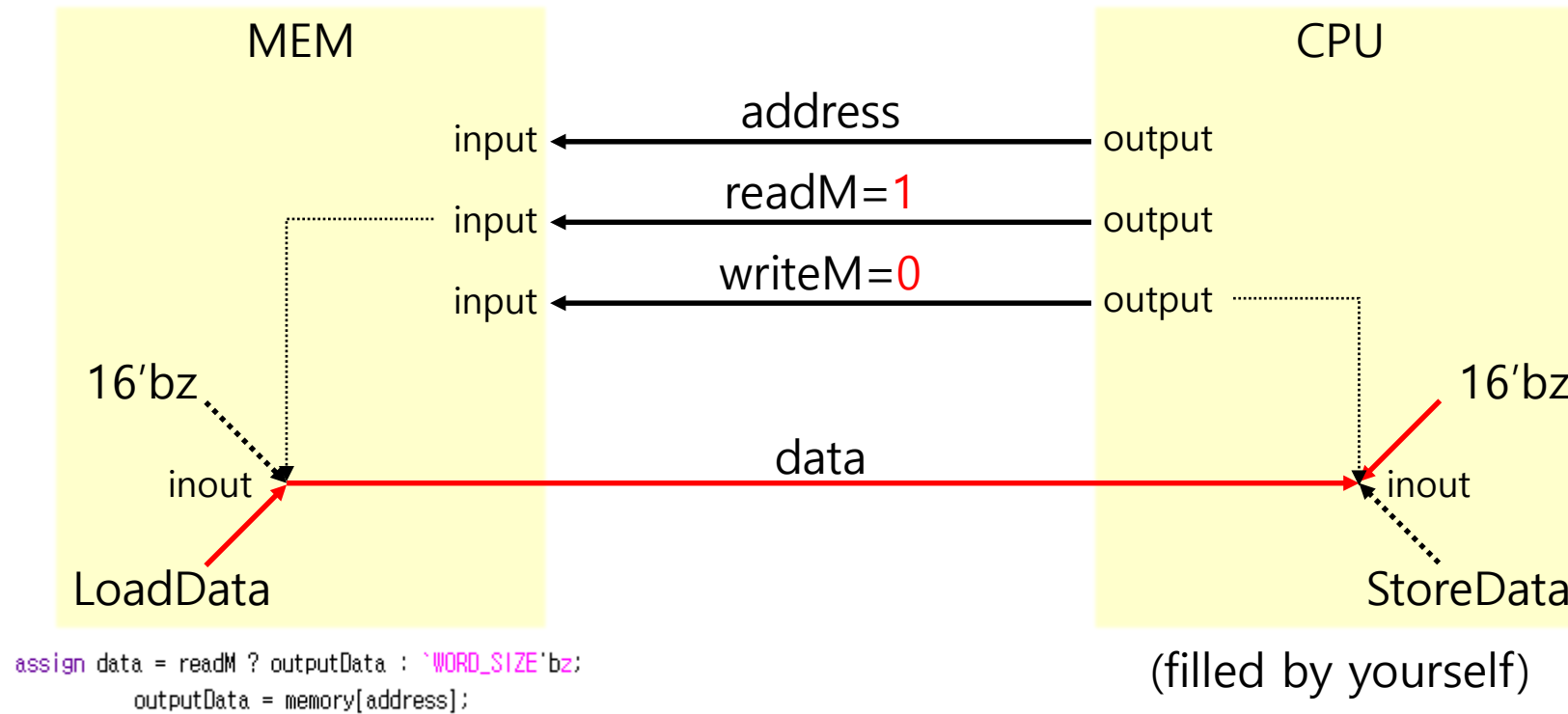


The memory puts data on the register, which is assigned to the inout port.

CPU-Memory interface – Store

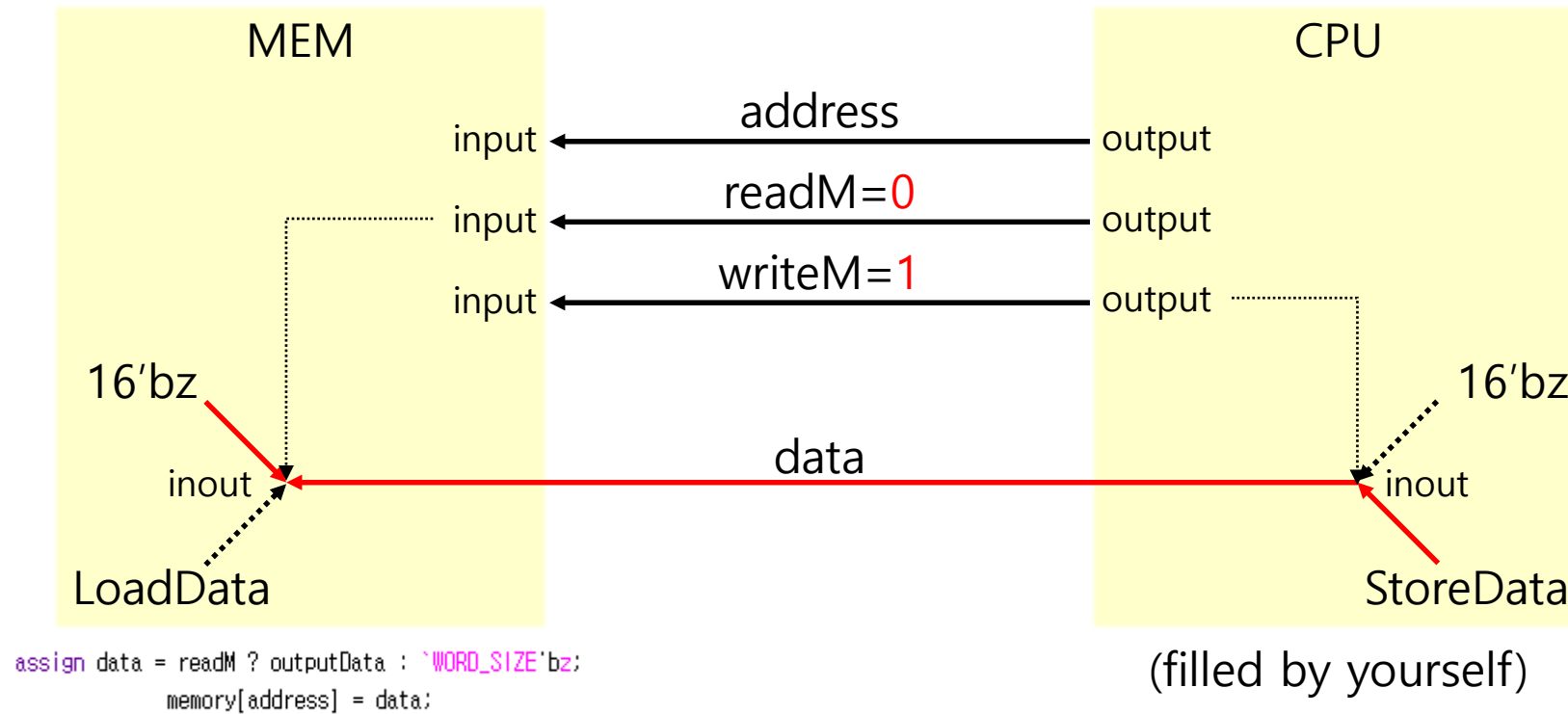

The memory puts 'z' on the inout port, and reads data from it.

CPU-Memory interface – Short Circuit

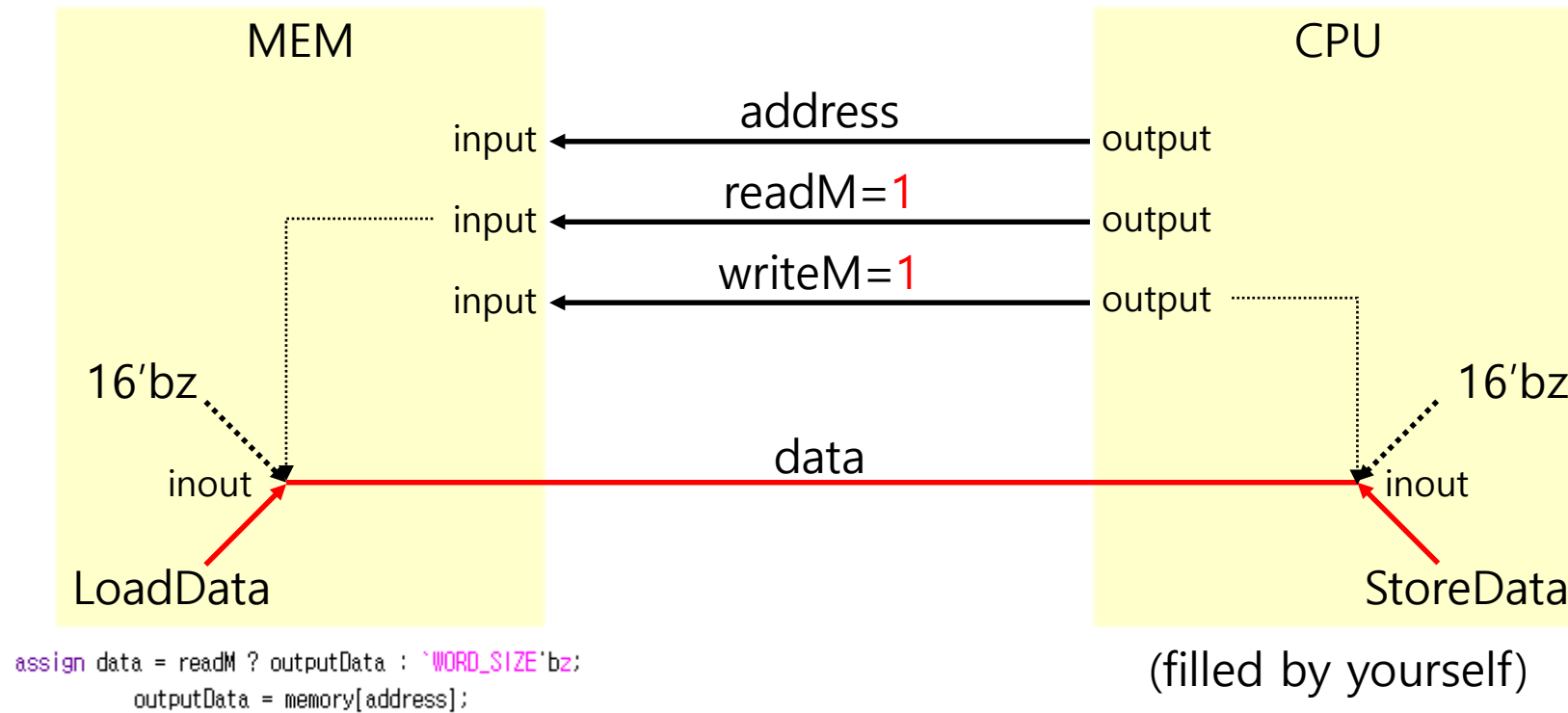

FORBIDDEN CASE: Both sides cannot write **SIMULTANEOUSLY**.

CPU-Memory interface

- **DO NOT FORGET** to turn the readM/writeM off before you use them again.
 - Otherwise, the memory will not respond to you.

```
// model the read process
assign data = readM ? outputData : `WORD_SIZE'bz;
always begin
    inputReady = 0;
    outputData = `WORD_SIZE'bz;
    #`PERIOD1;
    forever begin
        wait (readM == 1);
        #`READ_DELAY;
        outputData = memory[address];
        inputReady = 1;
        wait (readM == 0);
        outputData = `WORD_SIZE'bz;
        inputReady = 0;
    end // of forever loop
end // of always block for memory read
```

```
// model the write process
always begin
    #`PERIOD1;
    forever begin
        wait (writeM == 1);
        #`WRITE_DELAY;
        memory[address] = data;
        wait (writeM == 0); // wait for write pulse to go back to 0
    end // of forever loop
end // of always block for memory write
```

Assignment

- Implement a multi-cycle CPU.
 - It should support full TSC ISA.
- Due date: ~~4/26 23:59:59~~ 4/26 23:59:59
 - -10%/day penalty for late submissions until ~~5/3 23:59:59~~ 5/6 23:59:59
 - 0 point after ~~5/3 23:59:59~~ 5/6 23:59:59

Evaluation Criteria

- I'll offer you the testbench consisting of 56 tests.
- This will evaluate the functionality of your CPU
- The first 54 tests (TEST 1-1 to 19-2) validate the functionality of each individual instruction.
- The last two tests (TEST 19-3 and 20) validate the ability of executing streams of instructions.
- The "All Pass!" message shows that your CPU's functionality is **ALMOST SURELY PERFECT!**

Evaluation Criteria

- You can freely divide the execution into multiple stages.
 - You can break even "IF" or "ID" into several stages if you want.
- **But, the simpler instruction should have fewer stages.**
 - e.g., The JPR instruction is much simpler than the SWD instruction. Therefore, JPR must have fewer stages than SWD.
- You should remove the redundancies by reusing resources.
 - Please refer to the multicycle lecture note 15~17p
 - **Removing at least one redundancy is mandatory.**

Testbench Requirements

- You have to support three output ports for testbench:
 - num_inst : The number of instruction(s) executed
 - output_port : The value written by a WWD instruction
 - is_halted : 1 if and only if the CPU is halted by a HLT instruction.
 - This will stop the simulation and print the results.
- The value of those ports should be valid whenever a positive edge of the clock comes.

Thank You